

Embedded Systems Development

Exercise 1

1. Construct a microcontroller-based system to chase 5 LEDs one after another from left to right, repeatedly.

- a. If the system is supplied with 5V and an LED is driven with 2V and 15mA, what is the resistor required to limit the current to the LED?

.....

.....

.....

.....

.....

.....

- b. Prepare a BOM.

.....

.....

.....

.....

.....

- c. Draw the schematic diagram using a suitable schematic editor.

d. Draw the wiring diagram using Fritzing.

e. Write the required firmware in C and explain your code using comments in detail.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

2. Rewrite the firmware written for 1 (e) above making it more efficient.

[illegible]

- [illegible]

- Hint:* Use two BC547 transistors biased with $1\text{k}\Omega$ resistors to switch the GND line between first 5 and second 5 sets of LEDs.



Schematic diagram

Wiring diagram

This image shows a full page of a document template designed for handwriting practice or general writing. It consists of approximately 28 evenly spaced, horizontal dotted lines extending across the entire width of the page. The background is plain white, and there are no margins, headers, footers, or other markings present.